

## Homework 2

*Instructor: Robert Utterback**Due: September 15, 2017*

1. Draw logic diagrams for the following:

(a)  $Y = \overline{(A \cdot C)} + (A \cdot C)$

(b)  $Y = \overline{(C \cdot B)} + (A \cdot \bar{C})$

(c)  $Y = \overline{\bar{C} + B + A}$

2. Prove or disprove the following using truth tables.

(a)  $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$

(b)  $(A \cdot B) + A = A$

(c)  $\overline{A + B} = \overline{A} + \overline{B}$


3. Use the following truth table for the questions below:

Inputs		Outputs		
A	B	X	Y	Z
0	0	1	1	1
0	1	1	1	0
1	0	1	0	0
1	1	1	0	1

- (a) Write out the values of  $X$ ,  $Y$ , and  $Z$  as a product of sums.

- (b) Draw the PLA for the table above using the condensed (grid-like) notation.

4. Consider the following logic diagram:

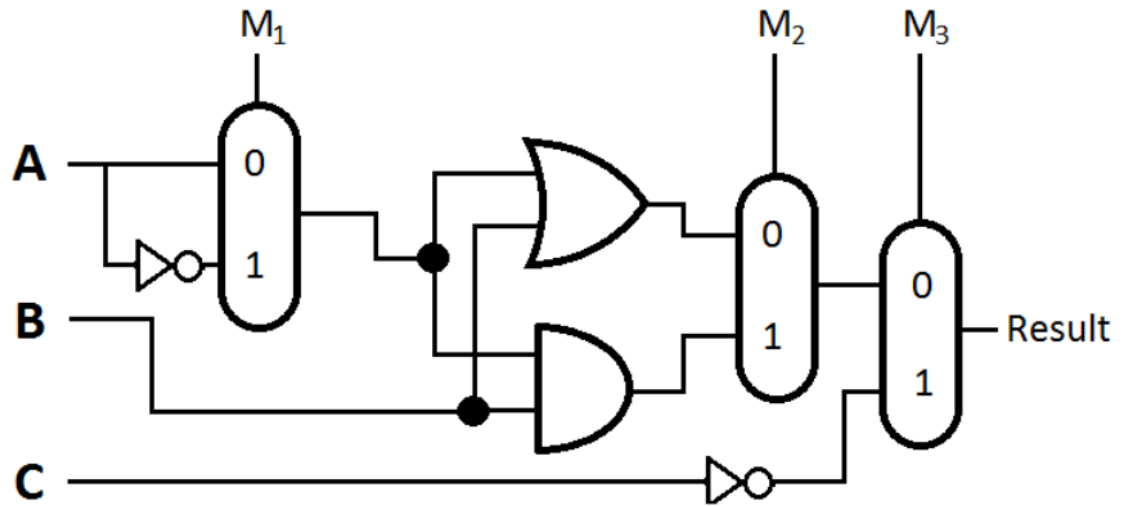

With the following inputs to the multiplexors, what is the logical representation in terms of  $A$ ,  $B$ , and  $C$ ?

(a)  $M_1 = 1, M_2 = 0, M_3 = 0$

(b)  $M_1 = 0, M_2 = 1, M_3 = 0$

(c)  $M_1 = 0, M_2 = 0, M_3 = 1$

5. Convert the following to binary and add. Assume an 8 bit signed adder (using two's complement).

(a)  $19 + 13$

(b)  $109 - 100$

(c)  $-42 + -117$

6. What is the longest chain of gates through a 4-bit ripple-carry adder? Through a 4-bit carry lookahead adder? Assume it takes two levels of gates (as in a PLA) to compute a sum bit, carry out bit, propagate bit or generate bit.